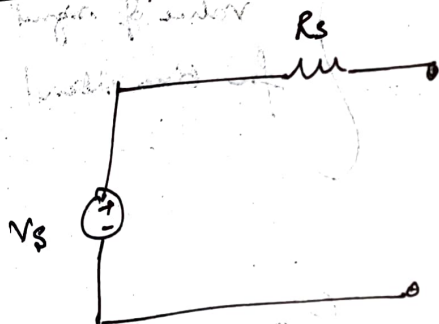



Device which converts
phys. signal to electronic signal

In courses we will primarily focus on the
transduced output, i.e., the electronic signal.


Methods of representing signals:




Voltage signal.

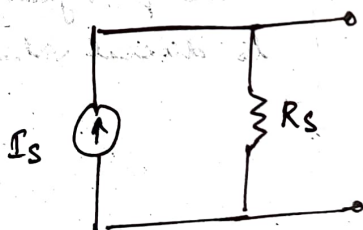

Current signal

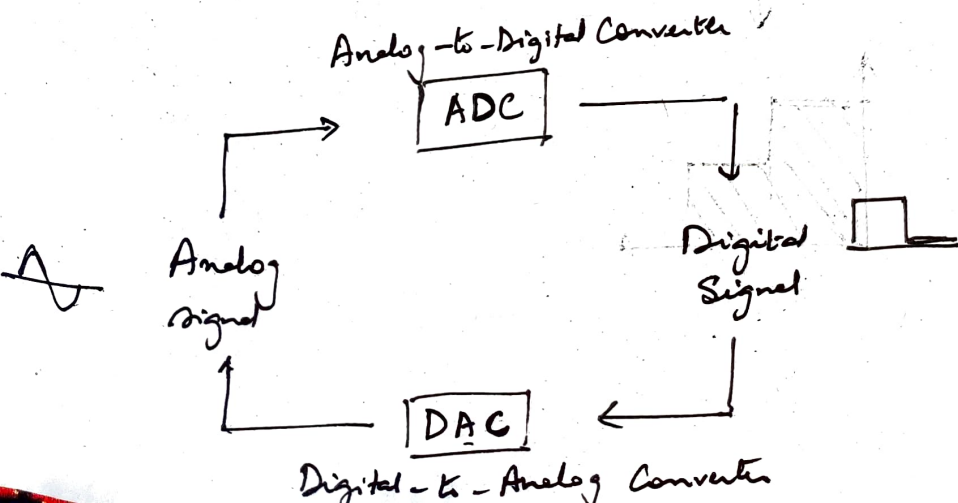


Converting from Analog to Digital:

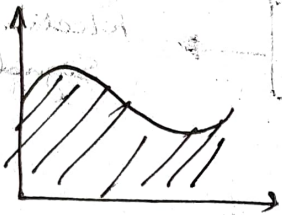


Sampling

Selecting discrete time intervals

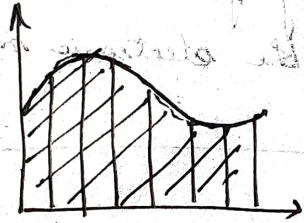



Approximation

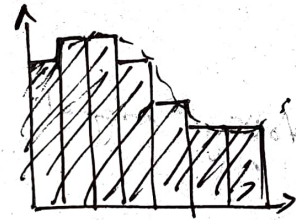Approximating the value of signal for time interval




Setting to discrete levels

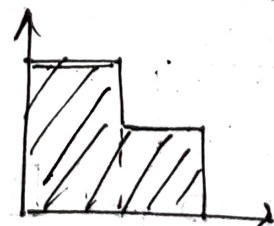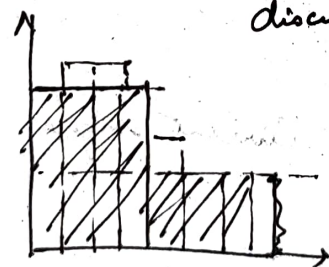Reducing/Increasing value of signals to discrete values



Amplifiers:

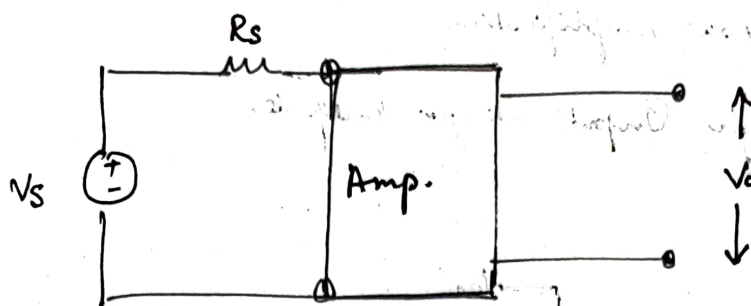


Generally, there are two types of amplifier.

① Linear: $\frac{dv_o}{dv_s} = A$ (Constant)

② Non-linear $\frac{dv_o}{dv_s} = f(v_s)$.

In this course, we will focus on only linear amplifier.

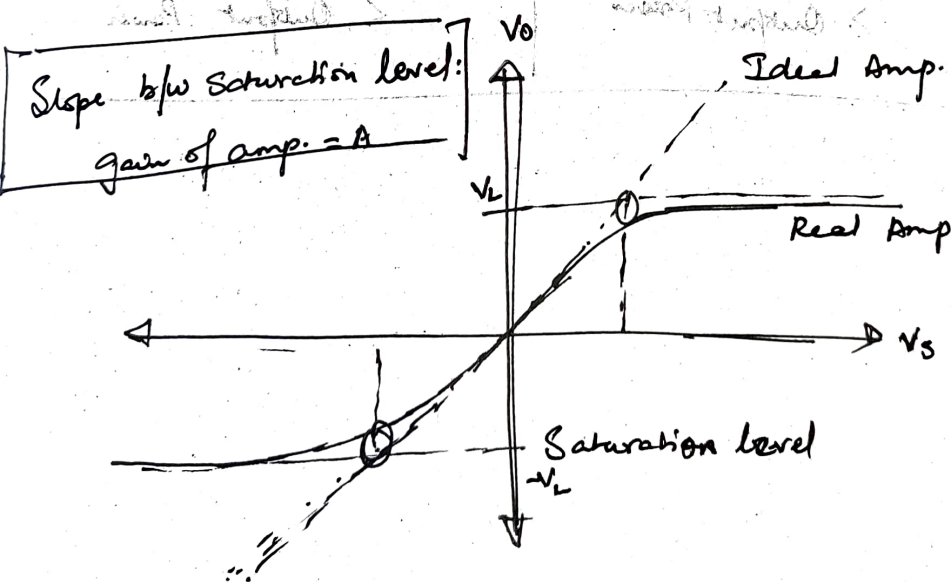Gain of Amplifier (A) = $\frac{V_o}{V_s}$




V_L is limited by power supply of the amplifier.



Properties:

- ① Linear Amplification
- ② Single Input single Output.

Symbol:

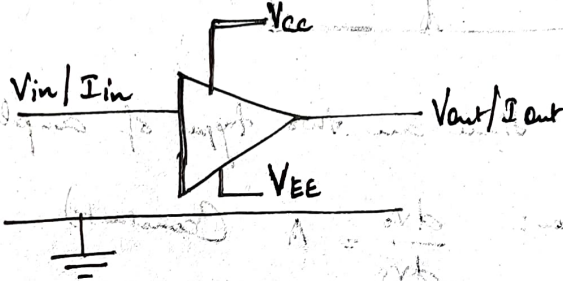


Transformer vs Amplifier

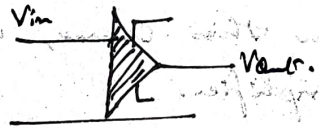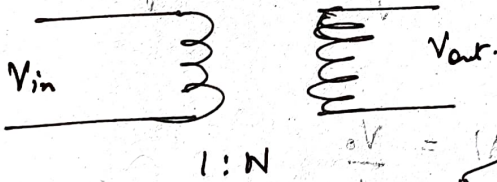

Input power
 \geq Output Power

Input power
 $<$ Output Power

Amplifier Circuit:

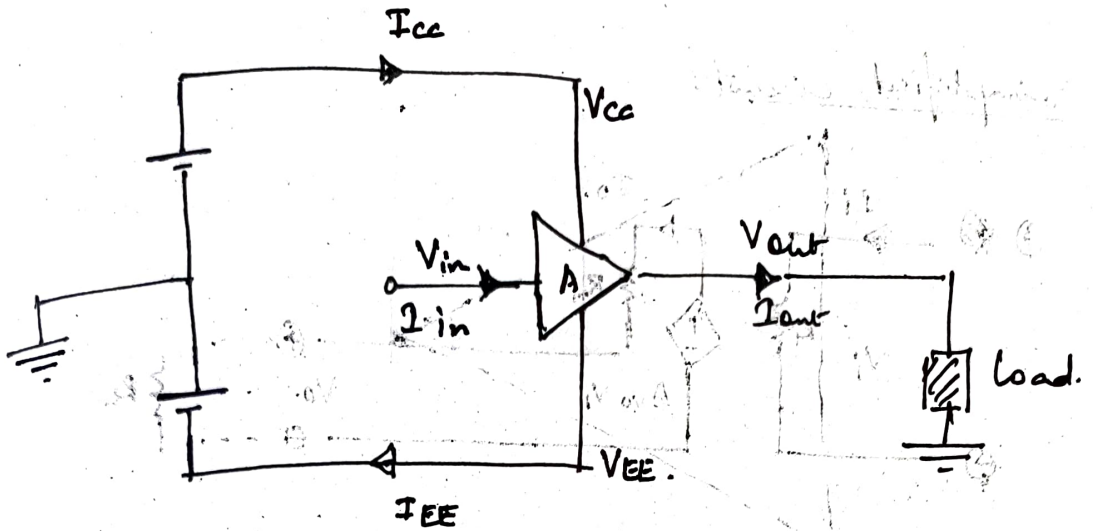

$$\frac{P_{out}}{P_{in}} > 1.$$

$$P_{in} + P_{DC} = P_{out} + P_{loss}$$


Assuming negligible losses,
efficiency of amplifier (η)

$$= \frac{V_L \cdot I_L}{P_{DC}} \approx 100\%$$

Where $P_{DC} = V_{CC} \cdot I_{CC} + V_{EE} \cdot I_{EE}$

Voltage Amplifier: (V_{in}, V_{out})


Simplified Circuit:

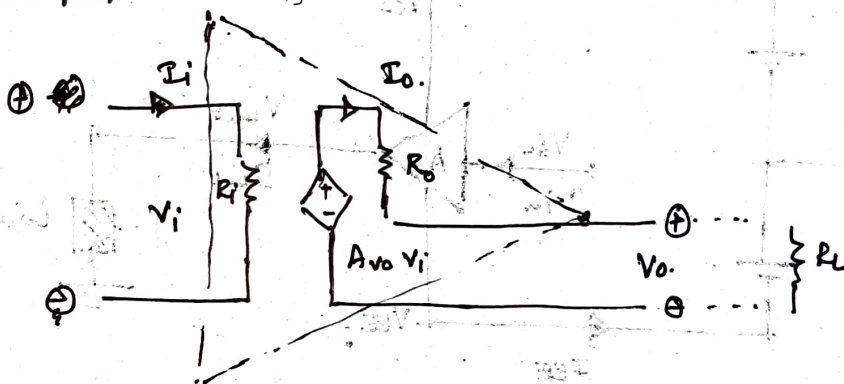

$$\text{Voltage gain} = \frac{V_o}{V_i} = A_{vo} \left[\frac{R_L}{R_o + R_L} \right]$$

for open circuit;
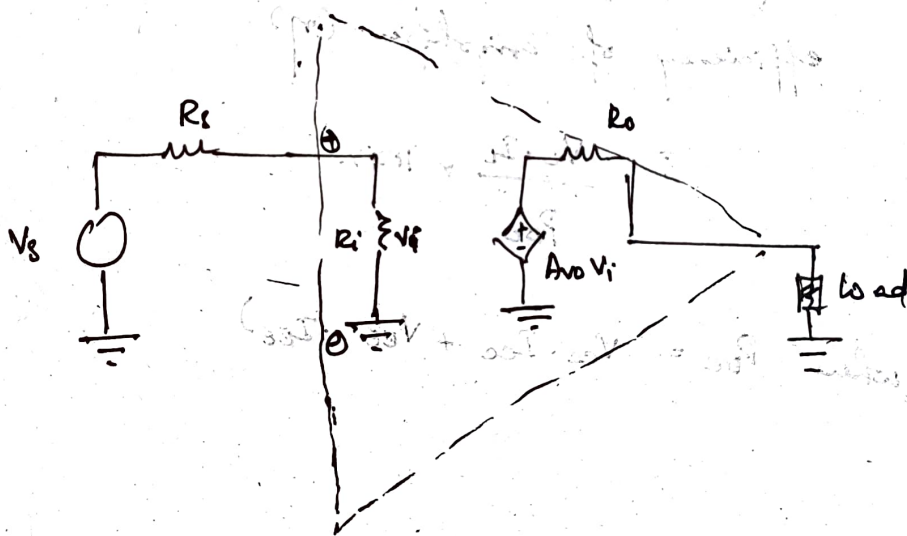
$$\text{gain} = \frac{V_o}{V_i} = A_{vo}$$



$$\text{Gain} = \frac{V_o}{V_s}$$

$$= A_{vo} \left[\frac{R_L}{R_o + R_L} \right] \left[\frac{R_i}{R_s + R_i} \right]$$

for greater efficiency

$$R_L \gg R_o \quad [R_o \rightarrow 0]$$

$$\text{and} \quad R_i \gg R_s \quad [R_i \rightarrow \infty]$$

Other type of Amplifiers:

① Current Amplifier:

$$\underline{I_{in}}: I$$

$$\underline{I_{out}}: I$$

② Transconductance / Transadmittance Amplifier:


$$\underline{I_{in}}: V$$

$$\underline{I_{out}}: I$$

③ Transresistance / Transimpedance Amplifier:


$$\underline{I_{in}}: I$$

$$\underline{I_{out}}: V$$

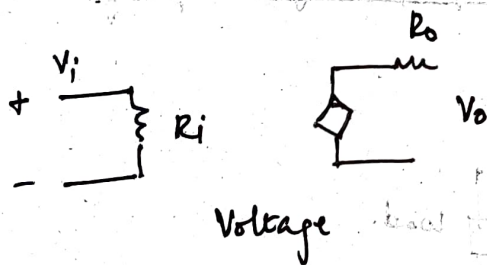


$$R_i \rightarrow \infty$$

$$R_o \rightarrow 0$$

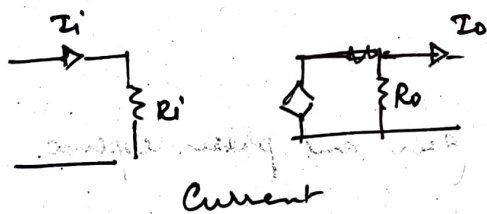


$$R_i \rightarrow 0$$

$$R_o \rightarrow \infty$$

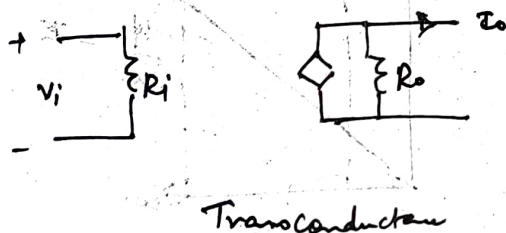

$$R_i \rightarrow \infty$$


$$R_o \rightarrow \infty$$

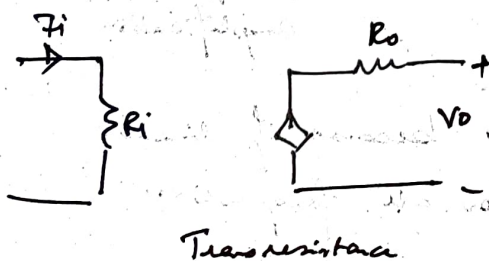

$$R_i \rightarrow 0$$

$$R_o \rightarrow 0$$

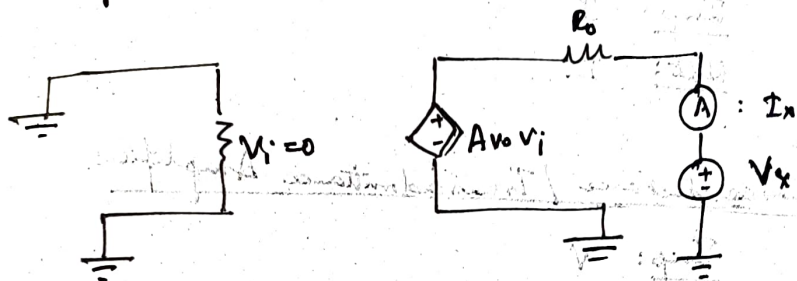
In a voltage amplifier, we can find the value of R_o by setting $V_i = 0$ and using a power source at output.





$$R_o = \frac{V_x}{I_x} \text{ at equilibrium.}$$

Characteristic of Amplifier by Frequency

Response:

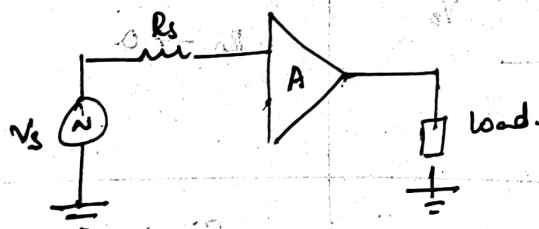

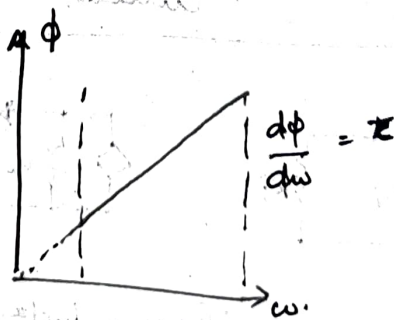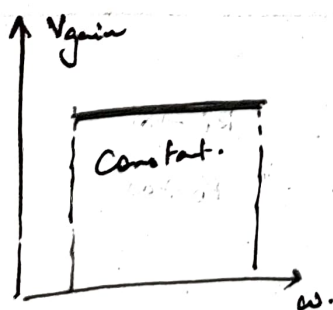
Bode plot: Plot of gain and phase response.



τ : delay b/c of amplification

the gain and delay because of linear amplifier is same for all frequencies.

Low-Pass filter:

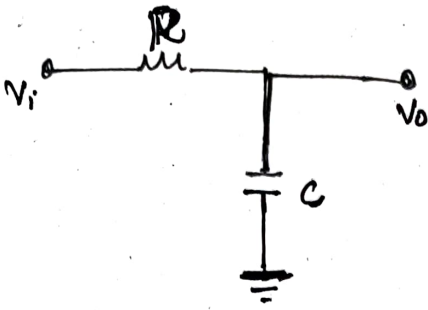

$$\begin{aligned}\text{When } \omega \rightarrow 0 \\ X_C \rightarrow \infty. \\ \Rightarrow V_o \approx V_i\end{aligned}$$

$$\begin{aligned}\text{When } \omega \rightarrow \infty \\ X_C \rightarrow 0 \\ \Rightarrow V_o \rightarrow 0.\end{aligned}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{|X_C|}{|X_C + R|} = \frac{(X_C)}{\sqrt{R^2 + (X_C)^2}} = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}$$

$$\text{where } \omega_0 = 1/RC.$$

$$\text{When } \omega \approx \omega_0 \quad \left| \frac{V_o}{V_i} \right| \approx \frac{1}{\sqrt{2}}, \quad \text{in dB: } -3 \text{ dB}.$$

$$\text{When } \omega \approx 10\omega_0 \quad \left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{10}} \approx \frac{1}{10}, \quad \text{in dB: } -20 \text{ dB}.$$

Phase change:

$$\angle \frac{V_o}{V_i} = \angle \frac{1}{1 + j\frac{\omega}{\omega_0}} = -\tan^{-1}(\omega/\omega_0)$$

Bode plot:

