

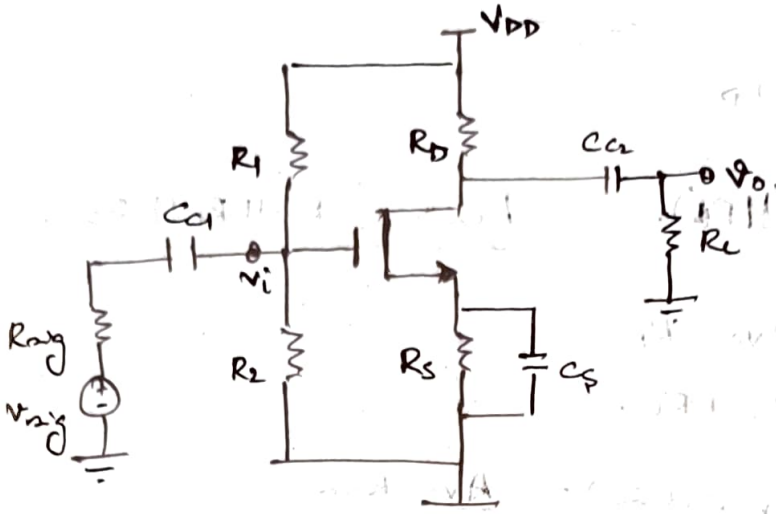


## Common Source Amplifier:

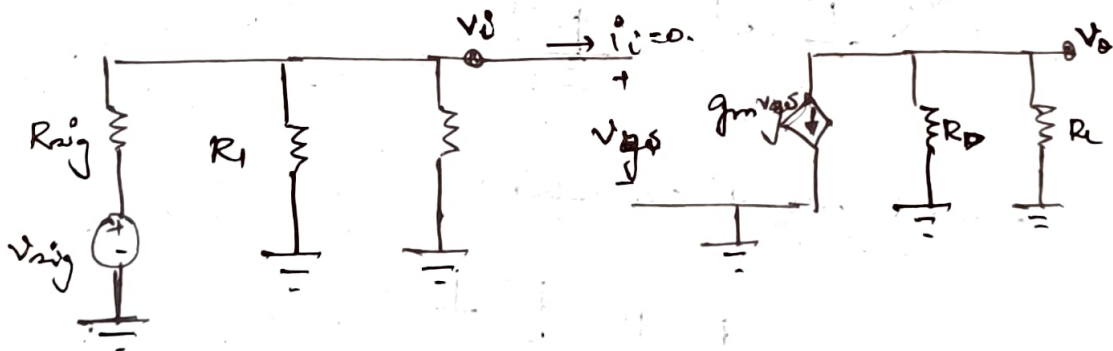

### Small Signal Equivalent Model:

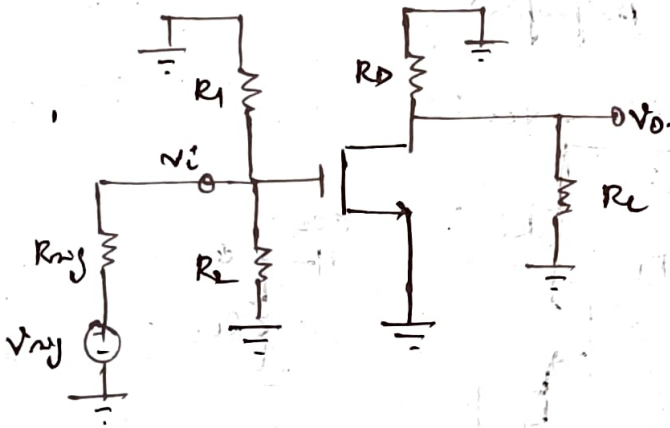

$$v_o = (-g_m v_{gs}) \times (R_D \parallel R_L).$$

When  $R_L \rightarrow \infty$ .

$$v_o = (-g_m R_D) v_i$$

$$\underline{\underline{= A_{vo} = -g_m R_D}}$$

$$\therefore i_i = 0 \Rightarrow R_i = \frac{v_i}{i_i} = \infty.$$

$$R_o = R_D.$$


$$R_{out} = (R_o \parallel R_L).$$

$$R_{in} = (R_1 \parallel R_2 \parallel R_3).$$


$$A_v = \frac{A_{vo} \cdot R_L}{R_o + R_L}.$$


$$G_v \text{ (voltage gain)} = \frac{A_v \cdot R_{in}}{R_{in} + R_{sig}}.$$

### Common Emitter Amplifier

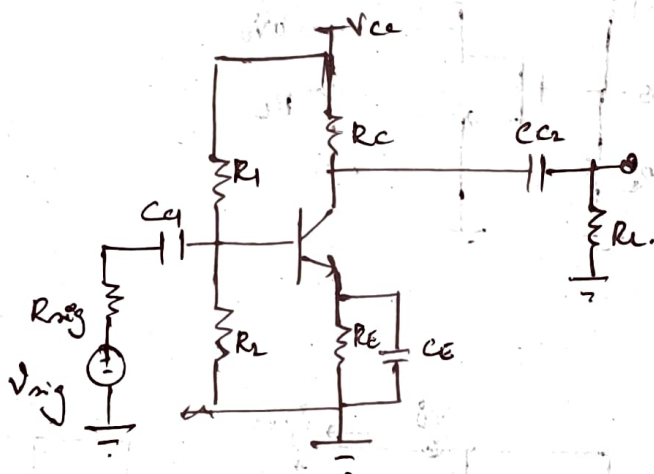

### Small signal equivalent

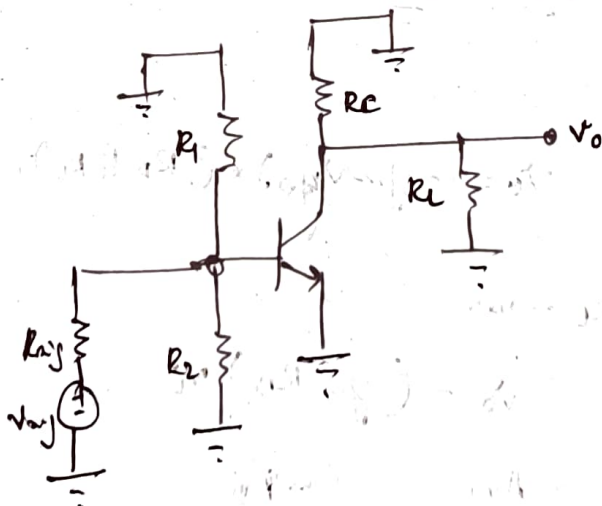

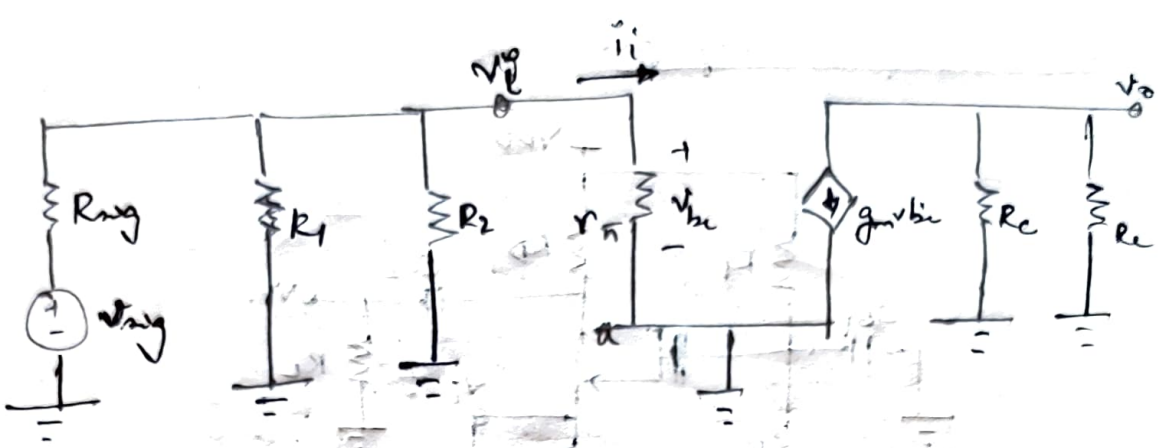

$$v_o = (-g_m v_{be}) [R_C \parallel R_L]$$

when  $R_L \rightarrow \infty$ ,

$$A_{vo} = - (g_m R_C)$$

$$R_o = R_C$$

$$R_i = \frac{v_i}{i_i} = r_{\pi}$$


$$A_v = \frac{A_{vo} R_o \parallel R_L}{R_o \parallel R_L + R_i}$$

$$R_{in} = (R_i \parallel R_1 \parallel R_2)$$



$$R_{out} = (R_o \parallel R_L)$$

$$G_v = \frac{A_v (R_{in})}{R_{in} + R_{sig}}$$

# Common Gate Amplifier

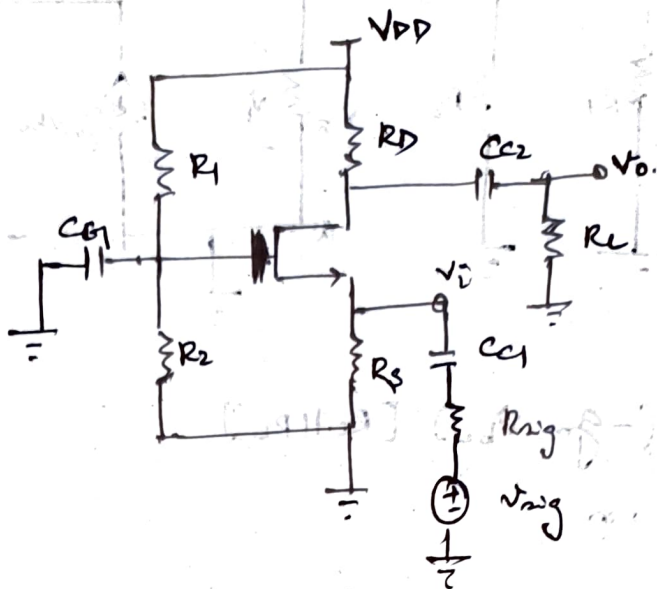

Small Signal Equivalent.

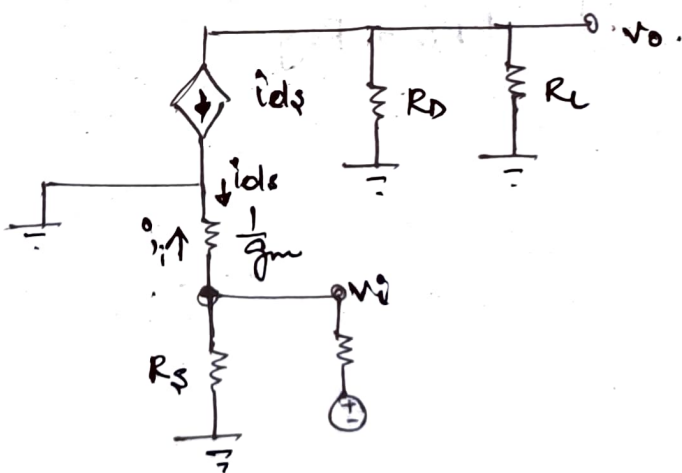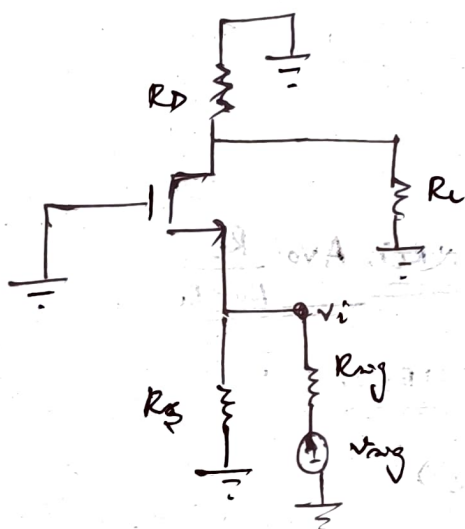

$$i_i = -i_{ds} = \cancel{g_m v_i} - g_m v_i$$

$$v_o = (-i_{ds}) (R_D \parallel R_L)$$

When  $R_L \rightarrow \infty$ .

$$v_o = g_m v_i R_D$$

$$\Rightarrow A_{v0} = \underline{g_m R_D}$$

$$\underline{R_i = 1/g_m} \rightarrow \text{Small value. Hence, not preferred}$$

$$\underline{R_o = R_D}$$


$$R_{in} = (R_i \parallel R_S)$$

$$A_v = \underline{A_{v0} \frac{R_L}{R_L + R_D}}$$



$$R_{out} = (R_o \parallel R_L)$$

$$G_v = \frac{A_v \cdot R_{in}}{R_{in} + R_{sig}}$$

### Common Base Amplifier

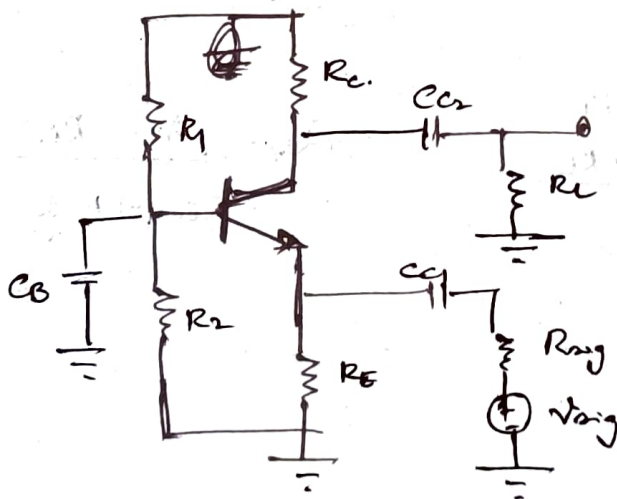

# Small Signal Equivalent Model.

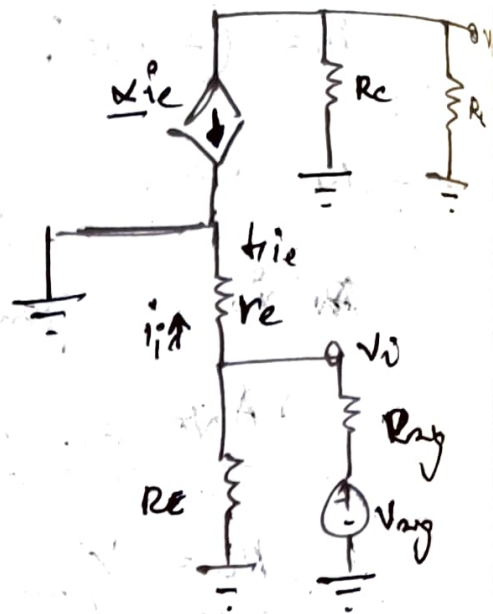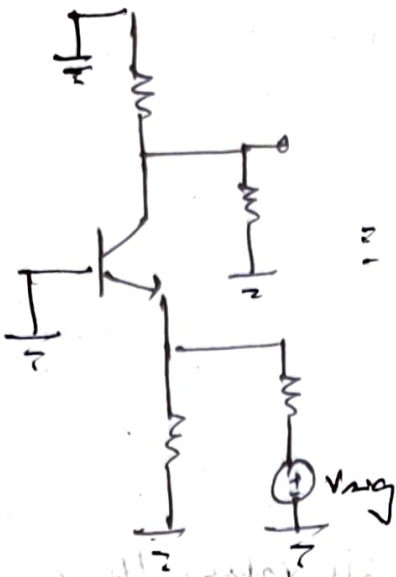

$$i_e = i_c = \frac{v_i}{r_e}$$

$$A_{vo} = (-\beta_i)(R_c \parallel R_L) = g_m(R_c \parallel R_L) v_i$$

When  $R_L \rightarrow \infty$ .

$$A_{vo} = g_m R_c$$

$$R_i = r_e = \frac{\alpha}{g_m}$$

$$R_o = R_c$$


$$A_v = \frac{A_{vo} \cdot R_L}{R_o + R_L}$$

$$R_{in} = (R_i \parallel R_E)$$



$$R_{out} = R_o \parallel R_L$$

$$G_v = \frac{A_v \cdot R_{in}}{R_{in} + R_{sig}}$$

# Common Drain Amplifier

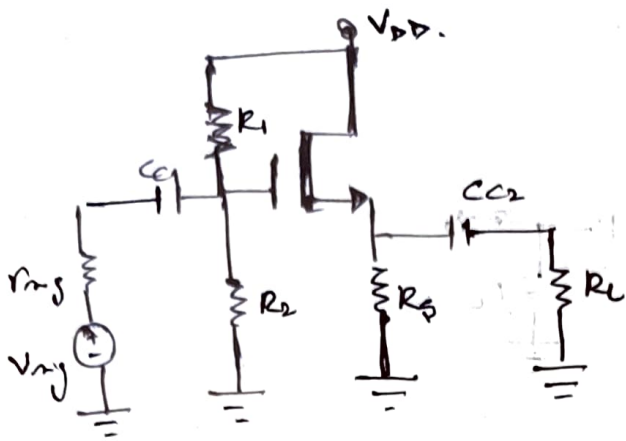

Small Signal Equivalent model.

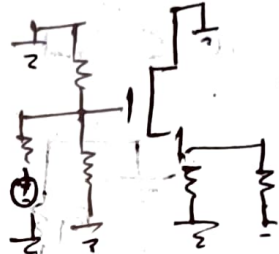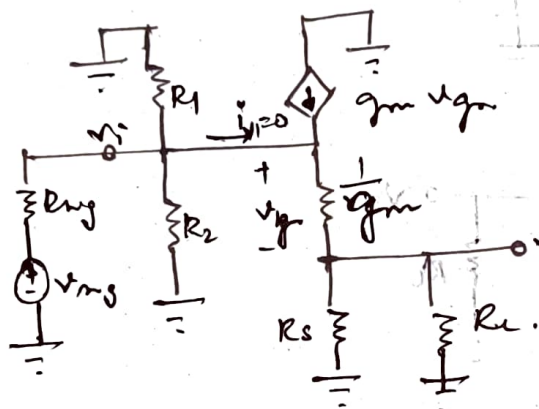

$$i_{R_L} = (g_m v_{gs})$$

$$v_o = i (R_S \parallel R_L)$$

$$v_i = i \left( \frac{1}{g_m} + (R_S \parallel R_L) \right)$$

$$\Rightarrow A_v = \frac{(R_S \parallel R_L)}{\frac{1}{g_m} + (R_S \parallel R_L)} = \frac{g_m (R_S \parallel R_L)}{1 + g_m (R_S \parallel R_L)}$$

$$R_o = 1/g_m, \quad R_i = \infty$$


$$A_{vo} = \frac{g_m R_S}{1 + g_m R_S} \quad R_{in} = (R_1 \parallel R_2)$$

$$R_{out} = (R_S \parallel R_L)$$



$$G_m = \frac{A_v \cdot R_{in}}{R_{in} + R_{sig}}$$



## Common Collector Circuit:

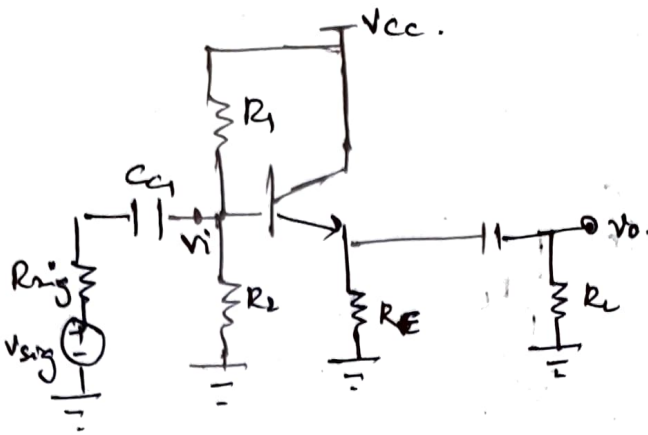

### Small Signal Equivalent Model.

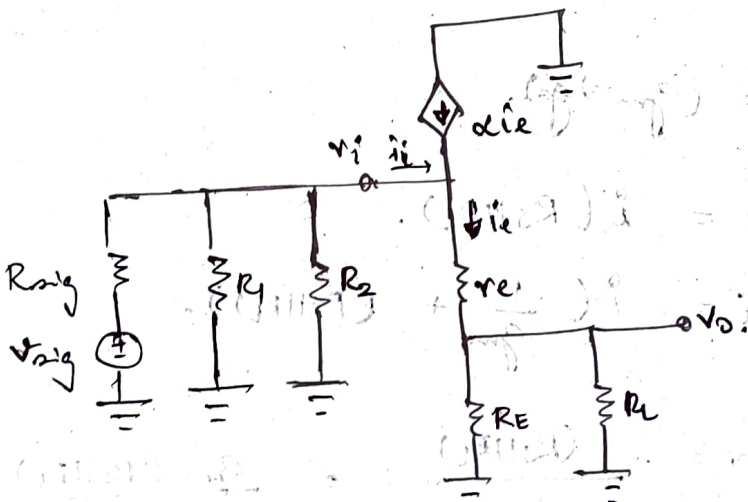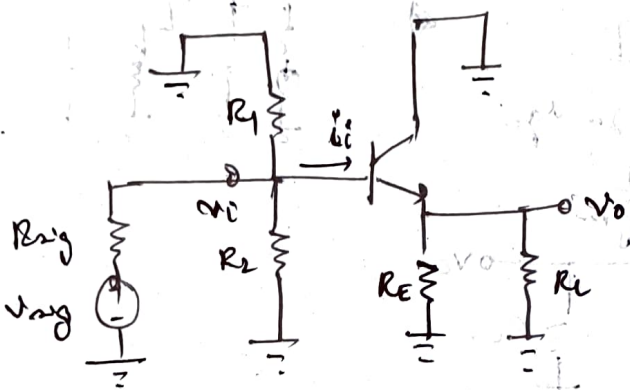

$$i_e = (\beta + 1) i_i$$

$$v_o = i_e (R_E \parallel R_L)$$

$$v_i = i_e (r_e + R_E \parallel R_L)$$

$$\frac{v_o}{v_i} = \frac{R_E \parallel R_L}{r_e + R_E \parallel R_L} = \frac{g_m R_E \parallel R_L}{1 + g_m R_E \parallel R_L}$$



$$R_o = r_e = \frac{\alpha}{g_m}$$

$$R_i = (\beta + 1) [r_e + (R_E \parallel R_L)]$$

$$R_{out} = (R_o \parallel R_E)$$

$$R_{in} = (R_i \parallel R_1 \parallel R_2)$$

$$A_v = \frac{A_v \cdot R_{in}}{R_{sig} + R_{in}}$$

Note:


In Common Collector (aka Emitter Follower) and Common Drain (aka Source Follower),

the gain is always  $< 1$ . In the ideal case of  $(R_S \parallel R_i) \rightarrow \infty$  or  $(R_E \parallel R_L) \rightarrow \infty$ ,

$$A_v = 1.$$

This kind of amplifier is used to generate a phase shifter with no gain.

## Current Mirror:

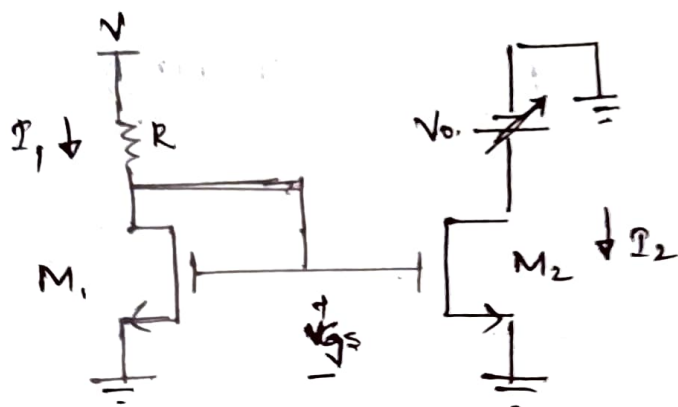

$M_1$  and  $M_2$  have Same  $k_n'$  and  $L$   
 Both are in Saturation mode  $\rightarrow$  and hence same  $V_{thn}$

$$I_1 = \frac{1}{2} k_n' \frac{W_1}{L} (V_{GS} - V_{thn})^2$$

For  $V_O > V_{GS} - V_{thn}$

$$I_2 = \frac{1}{2} k_n' \frac{W_2}{L} (V_{GS} - V_{thn})^2$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{W_1}{W_2}$$

When  $W_1 = W_2$   $I_1 = I_2$ .

This method is used to generate similar currents across multiple branches in an IC.

PS! If BJT's are used,

$$\frac{I_2}{I_1} = \frac{W_2}{W_1} \frac{1}{\beta(\lambda + 1) + 1} \quad \text{where } \lambda = \frac{A_2}{A_1}$$